

高階描述語言-有限狀態機(FSM)


陳韋達

Description of Vending Machine

- ❖一個簡易販賣機,上面有投幣、退幣、購買三個功能。
- ❖只允許5與10元硬幣投入,而所賣的飲料值25元
- ❖最多可以投到30元
- ❖一但購買產品,將自動找5元,並且致能(enable) 購買的訊號線,由邏輯"0"轉成"1"
- ❖當按下退幣,不論投入金額多少,都會將金額設 定為"0"元

Block of Vending Machine

Architecture

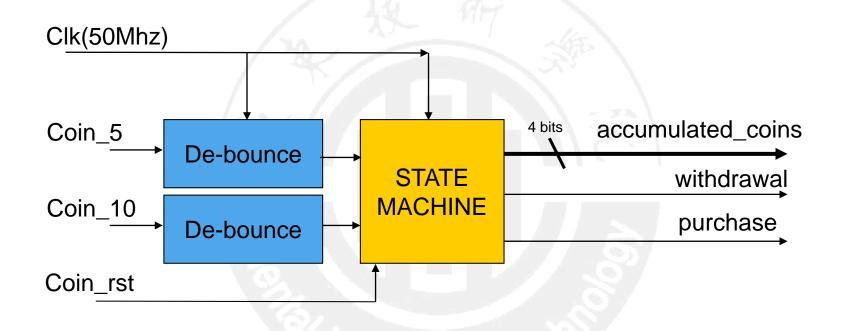

Vending machine(1)

```
vending_mach_testbench.coin_5

vending_mach_testbench.coin_10

vending_mach_testbench.coin_rst

vending_mach_testbench.clk

vending_mach_testbench.purchase

vending_mach_testbench.withdrawal

vending_mach_testbench.accumulated_coins[4:0]

x
0

5
15

25
0

10
15

20
0
```

```
module vending mach(coin 5,coin 10,coin rst,clk,
                    purchase, withdrawal, accumulated coins);
input coin 5,coin 10,coin rst,clk;
output purchase, withdrawal;
output [4:0]accumulated coins;
          purchase, withdrawal;
reg [4:0] accumulated coins, accumulated coins next;
reg [2:0] current state, next state;
always@(posedge clk)
 if(coin rst==1'b1 | purchase==1'd1)
   begin
     current state<=3'd0;
     accumulated coins <= 5'd0;
   end
 else
   begin
     current state
                      <=next state;</pre>
     accumulated coins <- accumulated coins next+accumulated coins;
    end
```


```
always@(coin 5 or coin 10 or current state or accumulated coins)
   case(current state)
       3'd0:if(coin 5==1'b1)
               begin
                  accumulated coins next=5'd5;
                  next state
                                        =1'd0;
                  purchase
                  withdrawal
                                        =1'b0:
               end
            else if (coin 10==1'b1)
               begin
                  accumulated coins next=5'd10;
                                        =3'd2;
                  next state
                  purchase
                                        =1'd0;
                  withdrawal
                                        =1'b0:
               end
            else
               begin
                                        =3'd0;
                  next state
                  accumulated coins next=5'd0;
                  purchase
                                        =1'd0:
                  withdrawal
                                        =1'b0;
               end
```

Vending machine(2)

```
3'd1:if(coin 5==1'b1)
       begin
           accumulated coins next=5'd5;
          next state
                                 =3'd2;
                                =1'd0;
           purchase
           withdrawal
                                =1'b0;
        end
     else if (coin 10==1'b1)
       begin
           accumulated coins next=5'd10;
          next state
                         =3'd3;
                              =1'd0;
          purchase
           withdrawal
                                 =1'b0;
        end
     else
       begin
           next state
                                =3'd1:
           accumulated coins next=5'd0;
          purchase
                                 =1'd0:
           withdrawal
                                 =1'b0:
        end
```

```
3'd2:if(coin 5==1'b1)
     begin
        accumulated coins next=5'd5;
                              =3'd3;
        next state
        purchase
                             =1'd0;
        withdrawal
                              =1'b0;
      end
   else if (coin 10==1'b1)
     begin
        accumulated coins next=5'd10;
        next state
                       =3'd4;
        purchase
                             =1'd0;
        withdrawal
                              =1'b0;
      end
     else
     begin
        next state
                              =3'd2:
        accumulated coins next=5'd0;
        purchase
                              =1'd0;
        withdrawal
                              =1'b0;
      end
```



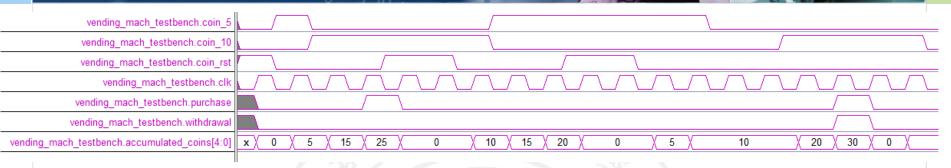

```
1. 須完成剩下
state 3~state5
的部分,
2. 撰寫測試檔
並觀察FSM的
波形是否正確。
```

```
3'd6:if(accumulated coins==5'd30)
              begin
                 accumulated coins next=5'd0;
                 purchase
                                      =1'd1;
                 next state
                                      =3'd0;
                 withdrawal
                                      =1'b1;
              end
           else
              begin
                 next state
                                      =3'd6:
                 accumulated coins_next=5'd0;
                 purchase
                                      =1'd0;
                 withdrawal
                                      =1'b0;
              end
      default:begin end
  endcase
endmodule
```

Test bench

```
module vending mach testbench;
                                                    initial
                                                      begin
          coin 5, coin 10, coin rst, clk;
req
                                                           20 coin 5=1'b1;coin 10=1'b0;coin rst=1'b0;
         purchase, withdrawal;
wire
                                                          20 coin 5=1'b0; coin 10=1'b1;
wire [4:0]accumulated coins;
                                                         # 20 coin 5=1'b0; coin 10=1'b1;
                                                         # 20 coin rst=1'b1;
vending mach U1(
                                                            ▲ 須完成剩下輸入資料的部分
                .coin 5 (coin 5),
                                                            ↓ 時間可以自行修改
                .coin 10 (coin 10),
                .coin rst(coin rst),


↓ 最後再加上$finish;

                .clk(clk),
                .purchase (purchase),
                .withdrawal (withdrawal),
                .accumulated coins(accumulated coins)
                );
initial
 begin
   clk=1'b0;
   coin 5=1'b0;
   coin 10=1'b0;
                                                          # 300 Sfinish;
   coin rst=1'b1;
                                                       end
                                                     endmodule
  end
initial
  forever #10 clk=~clk:
```


H.W.

❖設計、

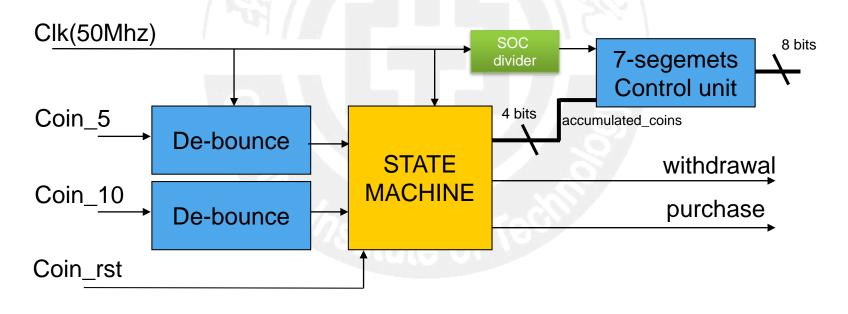
- 1.完成狀態機state 2~state5的部分
- 2.撰寫test bench
- 3.withdrawal與purchase輸出至LED
- 4.accumulated_coins的金額顯示至七段顯示器上



RTL view(1)

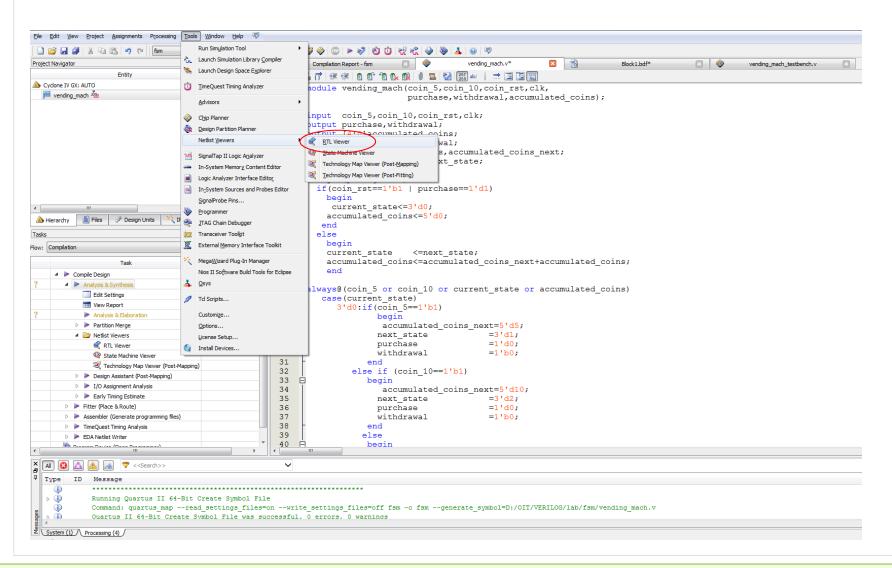

RTL view(2)

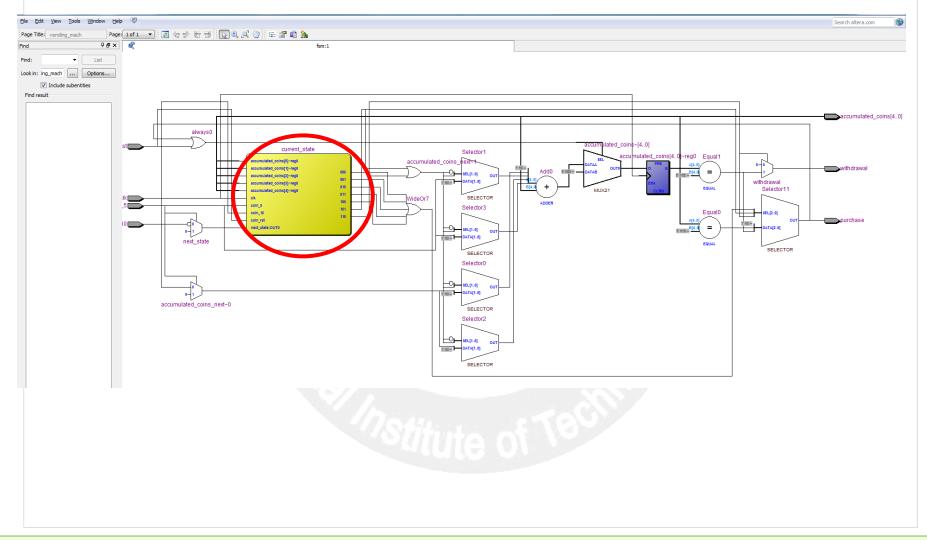

RTL view(3)

